

Con. 6758-11.


MP-4369

(3 Hours)

[Total Marks : 100]

**N.B. :** (1) Question No. 1 is **compulsory**.(2) Attempt any **four** questions out of remaining **six** questions.(3) **All** questions carry **equal** marks (**20 each**).

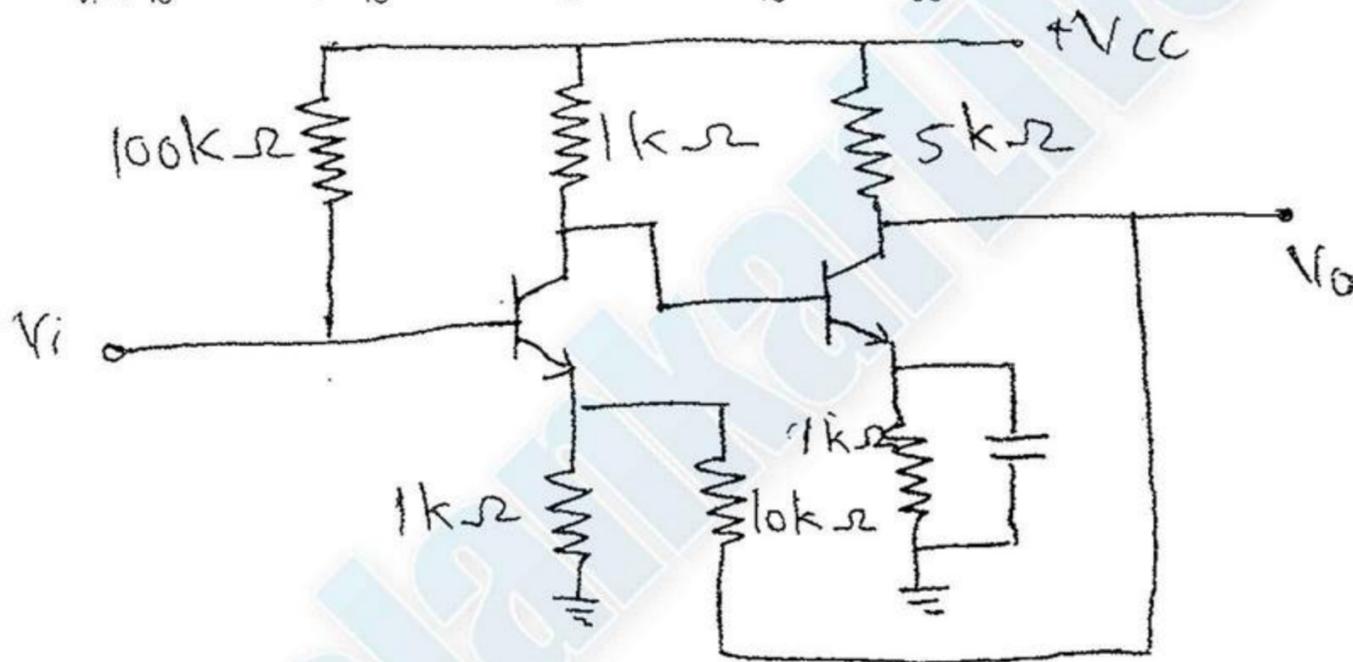1. (a) Compare linear and switched mode regulator in terms of efficiency, switching, losses, regulation, power handling capacity and size. 5
- (b) Write short note on transconductance amplifier. 5
- (c) Compare different classes of amplifier based on operating cycle, position on Q point and efficiency. 5
- (d) Difference between clipper and clamper. 5
2. (a) For circuit shown in **figure**, determine the type of feedback of the circuit,  $R_{if}$ ,  $R_{of}$  and  $A_{vf}$  ( $h_{ie} = 1 \text{ k}\Omega$ ,  $h_{fe} = 50$ , neglect the  $h_{re}$  and  $h_{oe}$ ). 10




- (b) Draw the block diagram of IC 723 and explain each block. 10
3. (a) Discuss Miller compensation and how it can be used to amplifier having unstable characteristics. 10
- (b) What is heat sink ? What is its function A BJT rated power of 15 W and a maximum junction temperature of  $175^\circ\text{C}$ . The ambient temperature is  $25^\circ\text{C}$  and the thermal resistance parameters are—  
 $\theta_{\text{snk-amb}} = 4^\circ\text{C/W}$  and  $\theta_{\text{cas-snk}} = 1^\circ\text{C/W}$ .  
 Determine the actual power than can be safely dissipated in the transistor. 10
4. (a) Draw and explain the working of Non-Inverting Op-amp. Derive the expression for its closed loop voltage gain. 10
- (b) Draw the circuit diagram for following with values of component using Op-amp. 10
  - (i) Inverting amplifier gain of 5.
  - (ii) Non-Inverting amplifier gain of 22.
  - (iii) Buffer amplifier.

[TURN OVER]

Con. 6758-MP-4369-11.

2

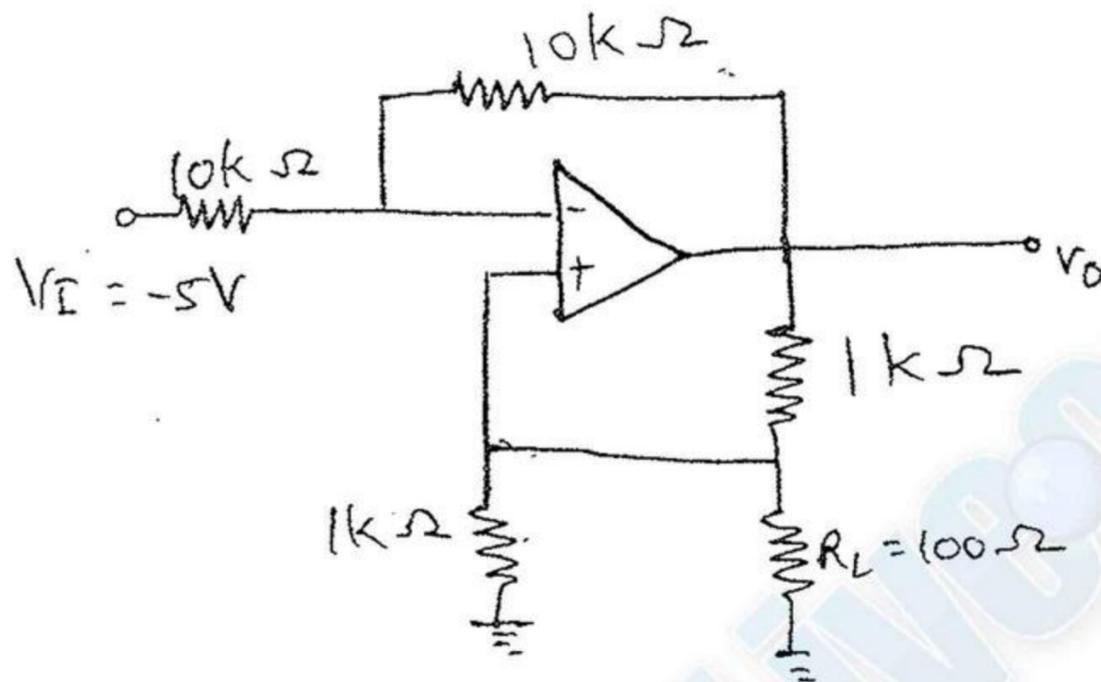5. (a) Design transformer coupled class A power amplifier to provide 5 W output to  $8 \Omega$  load. 12  
 (b) Determine load current in voltage to current converter. 8



6. (a) Draw the circuit diagram of colpitts oscillator. Derive expression for frequency of sustained oscillations. Determine condition to be satisfied for sustained oscillations. 10  
 (b) Draw and explain instrumentation amplifier using Op-amp. 10
7. Write short note on (any **two**) :— 20  
 (a) Practical Differentiator.  
 (b) Nyquist stability criteria.  
 (c) DC to DC converter.

DBEC DATA SHEET

Transistor type	Pdmax @ 25°C Watts	Icmax @ 25°C Amps	V <sub>CE</sub> <sup>(sat)</sup> volts	V <sub>CE0</sub> volts	V <sub>CE0</sub> (Sus) volts	V <sub>CE0</sub> (Sus) volts	V <sub>CE0</sub> volts	V <sub>BE0</sub> volts	D.C. current		Signal	h <sub>FE</sub>	V <sub>BE</sub> max.		
									min	max.				typ.	min.
2N3055	115.5	15.0	1.1	100	60	70	90	7	200	20	70	15	50	120	1.8
ECN055	50.0	5.0	1.0	60	50	55	60	5	200	25	100	25	75	125	1.5
ECN149	30.0	4.0	1.0	50	40	—	—	8	150	30	110	33	60	115	1.2
ECN100	5.0	0.7	0.6	70	60	65	—	6	200	50	280	50	90	280	0.9
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	220	125	220	260	0.9
2N525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	65	—	45	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	450	240	330	500	0.9

BFW 11—JFET MUTUAL CHARACTERISTICS

Transistor type	hie	hoe	h <sub>re</sub>	o/a	BFW 11—JFET MUTUAL CHARACTERISTICS											
					-V <sub>GS</sub> volts	I <sub>DS</sub> max. mA	I <sub>DS</sub> typ. mA	I <sub>DS</sub> min. mA	T <sub>J</sub> max.	I <sub>DSS</sub>	g <sub>mo</sub>	-V <sub>P</sub> Volts	r <sub>d</sub>	Derate		
BC 147A	2.7 K Ω	18 μ Ω	1.5 × 10 <sup>-4</sup>	0.4°C/mw	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0
2N 525 (PNP)	1.4 K Ω	25 μ Ω	3.2 × 10 <sup>-4</sup>	—	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1
BC 147B	4.5 K Ω	30 μ Ω	2 × 10 <sup>-4</sup>	0.4°C/mw	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0
					4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0

N-Channel JFET

Type	V <sub>DS</sub> max. Volts	V <sub>GS</sub> max. Volts	P <sub>d</sub> max. @25°C	T <sub>J</sub> max.	I <sub>DSS</sub>	g <sub>mo</sub>	-V <sub>P</sub> Volts	r <sub>d</sub>	Derate
2N3822	50	50	300 mW	175°C	2 mA	3000 μΩ	6	50 KΩ	2 mW/°C
BFW 11 (typical)	30	30	300 mW	200°C	7 mA	5000 μΩ	2.5	50 KΩ	—

UJT type	P <sub>d</sub> max. @25°C	I <sub>E</sub> max. @25°C	I <sub>P</sub> peak pulse current	V <sub>BE</sub> Volts max.	T <sub>J</sub> max.	η	R <sub>BB</sub> KΩ	Max. I <sub>P</sub> μA
2N2646	300mW	50mA	2Amp.	30	125°C	0.56	4.7	9.1