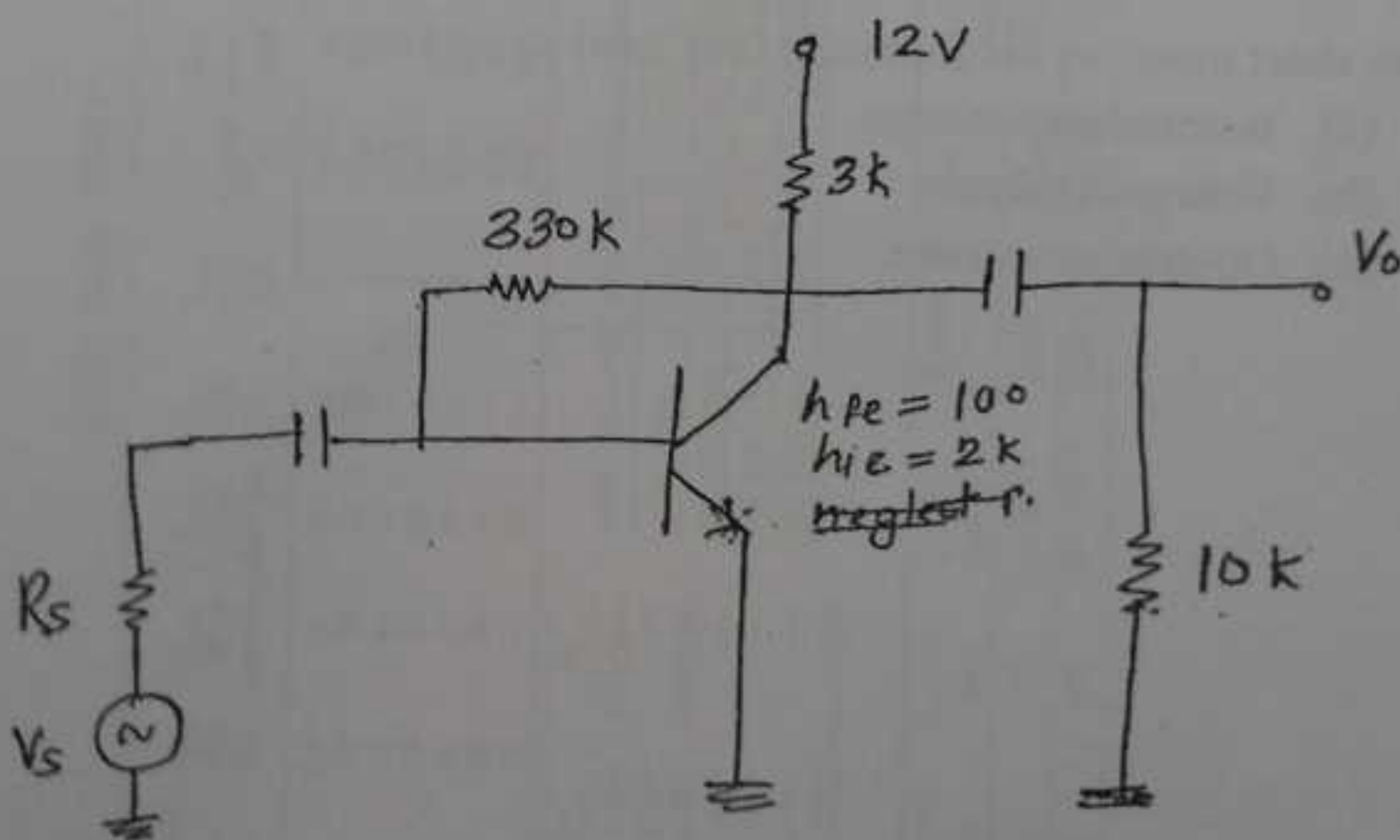


- N.B. : (1) Question No.1 is compulsory.
 (2) Attempt any four questions out of remaining six questions.
 (3) Assume suitable data if required.



1. (a) State and explain Barkhausen criterion. 5
 (b) Differentiate class A and B power amplifier 5
 (c) Explain concept of virtual ground. 5
2. (a) Design class A power amplifier to provide 2 W power to the speaker of 40 W. 12
 (b) Design a regulated power supply which will output +5 and -5 voltage. 5
3. (a) Compare the different types of negative feedback. 10
 (b) Determine A_{vf} , R_{if} , R_{of} using -ve feedback approach. 10



4. (a) Design a linear combination of circuit using Op-amp to combine three sig and give 10 output as, $V_0 = -2V_1 - 8V_2 - V_3$. All resistance values should be $\leq 200 K$.
- (b) In an integrator circuit $R_1 = 500 \Omega$, $R_f = 5K$, $C = 0.1 \mu f$. If i/p signal period is 10 $T = 0.5 ms$. Then find the frequencies f_a and f_b . Also comment whether the circuit can work as an integrator. Mark f_a and f_b on integrator frequency response.

Con. 7830-KR-7259-12.

2

5. State the circuit that can be used for the given application. Draw its circuit diagram and explain it – 20
- (a) A circuit which rectifies sine wave in mv amplitude.
 - (b) A circuit which generates a sine wave signal of fixed frequency.
 - (c) A circuit used to convert any form of the signal into a square wave.
 - (d) A circuit which subtracts two signals.
6. (a) Derive max possible efficiency for class B transformer coupled power amplifier at max power O/P. 10
- (b) Design a suitable heat sink for the following applications :- 10
- Transistor – ZN 3055
- Actual power dissipation in transistor = 50 W
- Thermal resistance case to heat sink = $\theta_{C-H} = 0.5 \text{ } ^\circ\text{C/W}$.
- Ambient temperature = 40 $^\circ\text{C}$
7. Write short notes on the following (any two) :- 20
- (a) Instrumentation amps.
 - (b) Voltage regulators
 - (c) Op-amp parameters.
-