



(3 Hours)

[ Total Marks : 100  
AE

N.B. : (1) Question No. 1 is **compulsory**. Attempt any **four** from remaining **six** questions.

(2) **Illustrate** your answers with **block diagrams** and **circuit diagrams**.

1. (a) Explain the terms Threshold and Resolution. 5
- (b) How are Lissajous patterns used for phase and frequency measurements. 5
- (c) What are the factors involved in selection of a voltmeter ? 5
- (d) Describe briefly the Non-fade display system. 5
2. (a) Explain in detail working of True RMS responding voltmeter. 10
- (b) Find the response of first order system to step input. 10
3. (a) Describe the working of dual slope integrating type Digital Voltmeter. 10
- (b) Explain in detail the working of a digital Multimeter. 10
4. (a) Describe the working of inverted R-2R Ladder digital to Analog convertor. 10
- (b) Describe in detail the working of Analog phase meter. 10
5. (a) What is Period measurement and Ratio measurement in a digital Frequency meter. 10
- (b) Explain the function of delay line and trigger circuit in a cathod Ray Oscilloscope. 10
6. (a) Explain in detail a Sampling CRO. 10
- (b) Explain the working of a Function Generator. 10
7. Write short notes on any **three** of the following :— 20
  - (a) Effect of Zeta ( $\xi$ ) on Second Order System
  - (b) Touch Screen Display System
  - (c) Data Acquisition System
  - (d) Intensity Modulation in a CRO.

[ TURN OVER