

(3 Hours)

- N.B. : (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of remaining six questions.
 (3) Figures to the right indicate full marks.



1. (a) State the performance characteristics of DVM. 5
 (b) Draw and explain peak reading voltmeter 5
 (c) Explain ink-jet writing system. 5
 (d) What is LCD display system ? 5

2. (a) What are lissajous patterns ? Explain with suitable diagrams how it can be used for measurement of frequency and phases state the limitations. 10
 (b) Draw and explain multi-channel data acquisition system. 10

3. (a) Explain with diagram working of successive approximation type DVM state advantages and limitations. 10
 (b) What is Period Measurement and Ratio Measurement in a digital frequency meter ? 10

4. (a) Describe in detail analog phase meter. 10
 (b) Find the response of first order system to step and ramp input. 10

5. (a) Draw the block diagram of dual trace C.R.O. and explain each block. 10
 (b) Explain R-2R ladder technique of digital to analog conversion. 10

6. (a) Draw and explain function generator with diagrams. 10
 (b) Explain following w.r.t. CRO - 10
 - (i) Post deflection acceleration
 - (ii) ALT/CHOP
 - (iii) Triggering
 - (iv) Focus and Intensity
 - (v) Time/Div and Volts/Div.

7. Write short notes on (any three) :- 20
 - (a) Intensity and velocity modulation
 - (b) Dual slope integrating type DVM
 - (c) Multimeter
 - (d) True RMS voltmeter.