

Con. 2960-09.

(OLD COURSE)

(3 Hours)



N.B. : (1) Question No. 1 is compulsory.
(2) Attempt any four out of remaining six questions.

1. (a) Explain the differences between combinational and sequential circuits. 5
(b) Give comparison of various logic families. 5
(c) What are the hazards in combination logic circuits ? Explain with suitable example. 5
(d) What is multiplexer ? Draw and explain 4 : 1 MUX using logic gates. 5
2. (a) Convert following numbers : 8
(i) $(89.75)_{10} \longrightarrow (?)_8$
(ii) $(12345)_{10} \longrightarrow (?)_{16}$
(iii) $(23.23)_8 \longrightarrow (?)_{16}$
(iv) $(ABAB.1F)_{16} \longrightarrow (?)_2$
(b) Perform following operations :- 8
(i) $73 - 10$ using 2's complement method
(ii) $10 - 73$ using 2's complement method
(iii) $9 - 3$ using 9's complement method
(iv) $3 - 9$ using 9's complement method.
(c) What is gray code ? Explain one applicaiton of gray code. 4
3. (a) Why NAND and NOR gates are referred as universal gates ? Implement X-NOR 10
gate using only NAND gates and only NOR gates.
(b) Show that
$$\frac{A\bar{B} + ABC + A(B + \bar{A}B)}{A\bar{B} + ABC + A(B + \bar{A}B)} = A\bar{B}$$
 5
(c) Show that - 5
$$AB + \bar{A}C = AB + \bar{A}C + BC$$
4. (a) Simplify and Implement using logic gates - 10
 $f = \Sigma (2, 5, 7, 15) + D (6, 9, 13)$
(b) Simplify using Quine-McCluskey method 10
 $f = \Sigma (2, 3, 6, 7, 8, 9, 10, 12) + D(13).$
5. (a) Design Binary to Gray code converter. 10
(b) Design full adder using logic gates. 10
6. (a) Convert SR flip-flop to D flip-flop. 10
(b) Design MOD-10 asynchronous Ripple counter. 10
7. (a) Design MOD-5 synchronous counter using JK flip-flop. 10
(b) What is Ring counter ? Design Ring counter using D-flip-flop. 10