

Con. 6786-11.

**MP-4366**

(3 Hours)

[Total Marks : 100

- N.B. :** (1) Question No. 1 is **compulsory**.  
 (2) Attempt any **four** questions from the remaining **six** questions.  
 (3) Assume **suitable** data wherever **necessary**.

1. (a) Convert  $(782.56)_{10}$  to :— 4  
 (i) BCD      (ii) Hexadecimal      (iii) Octal      (iv) Binary.
- (b) Do the following arithmetic operation :— 4  
 (i)  $(742.23)_8 + (32.15)_8$   
 (ii)  $(7AD.5C)_{16} - (15D.2A)_{16}$  use 16's complement  
 (iii)  $(523.6)_{BCD} + (728.9)_{BCD}$   
 (iv)  $(11001.101)_2 - (1011.01)_2$  use 1's complement
- (c) Derive characteristic equation of JK Flip Flop. 4
- (d) State and prove De Morgan's theorem. 4
- (e) Explain how two half subtractors can be connected to form full subtractor. 4
  
2. (a) Reduce the following using KMap and implement using NAND gates. 10  
 (i)  $f(A, B, C, D) = A\bar{B} + AB\bar{C}D + C\bar{D} + B$   
 (ii)  $y(A, B, C, D) = \pi M(0, 2, 4, 5, 8, 9, 10, 12)$
- (b) Implement the expression :— 10  

$$y = A\bar{B} + CD + ABC\bar{C} + B\bar{C}D$$
 using (i) Single 8 : 1 MUX and gates.  
 (ii) 4 line to 16 line decoder and gates.
  
3. (a) What is the difference between synchronous and asynchronous counters ? 10  
 Design a three bit up-down synchronous counter using JK Flip Flop.
- (b) Reduce the following Boolean expression using Boolean laws and implement using NAND gates. 10  
 (i)  $y = \bar{A}(A + \bar{B})(A + \bar{C})(\bar{A} + B) + \bar{C}(C + \bar{A}\bar{B})$   
 (ii)  $y = \overline{\overline{A\bar{B} + \bar{C}} + A + B}$   
 (iii)  $y = \overline{\bar{A}BC} + \overline{(\bar{B} + \bar{C})}\bar{A}$   
 (iv)  $\overline{A \cdot \bar{B} \cdot C} + BC$
  
4. (a) What is race around condition in JK Flip flop ? Explain Master Slave JK Flip Flop and show the problem of race around condition avoided in MS-JK Flip Flop. 10
- (b) Compare TTL and CMOS logic families. Draw the TTL NAND gate and explain the totem pole output. 10

**[TURN OVER**

Con. 6786-MP-4366-11.

2

5. (a) Design a 2 bit comparator using gates. Show the truth table. K Map and steps for Design. 10
- (b) Explain the different types of shift registers. Using serial in serial out shift register draw a ring counter. 10
6. (a) Design a BCD to seven segment decoder for common Cathode type of display. Use gates for design. 10
- (b) Reduce the following function using Quine Mc Clusky Algorithm. 10
- $$f(A, B, C, D) = \sum m(0, 1, 2, 5, 6, 7, 8, 9, 10, 12, 15)$$
7. (a) Explain the rules for BCD addition. Design a BCD adder using IC 7483 and gates. 10
- (b) Explain any two :— 10
- (i) ALU
  - (ii) Hamming Code
  - (iii) Diode ROM.

—————V—————