
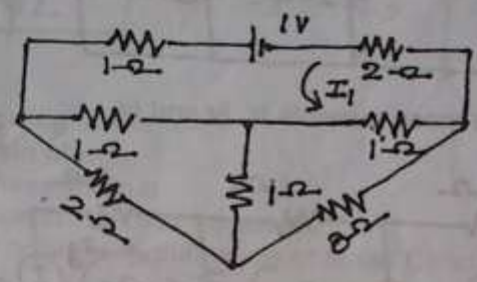


- N.B. (1) Question No.1 is compulsory.
 (2) Attempt any four questions out of the remaining six questions.
 (3) Assume any suitable data if required.
 (4) Figures to the right indicate full marks.

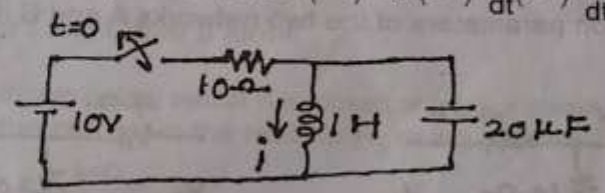
1. (a) Check the following function for Hurwitz using Routh array method :— 5
 $F(s) = s^4 + 8s^3 + 4s^2 + 2s + 8.$
 (b) Draw dual of a given network :— 5




- (c) For a given network switch K is closed and a steady state is reached in the network. 5
 At $t=0$, the switch is opened. Find $i(0^+)$, $V_c(0^+)$, $\frac{di}{dt}(0^+)$, $\frac{d^2i}{dt^2}(0^+)$



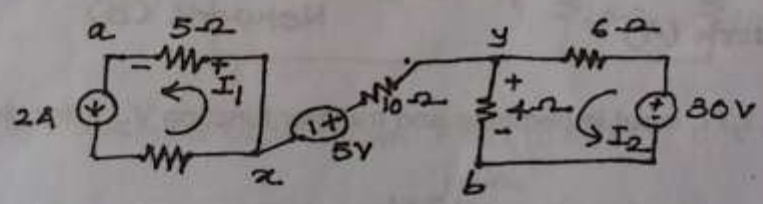- (d) Find the voltage V_{ab} in the network shown — 5



2. (a) Using mesh analysis find the voltage across the capacitor — 15

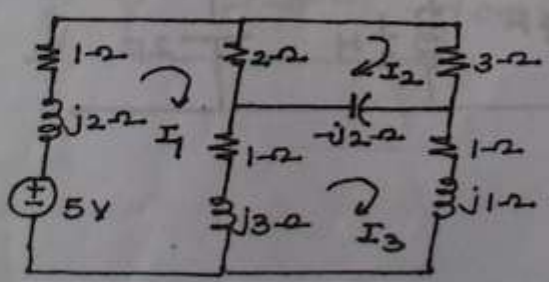


Con. 5534-SP-7394-09.

(b) Test the following functions for positive realness —


(i) $\frac{s^2 + 2s + 1}{s^2 + 4s + 4}$

(ii) $\frac{2s^2 + 2s + 1}{(s^2 + 1)^2}$

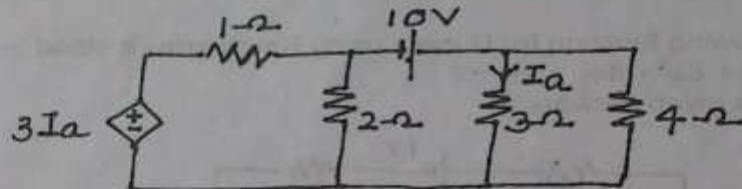
3. (a) Find the current through 4 Ω resistance using Thevenin's theorem —



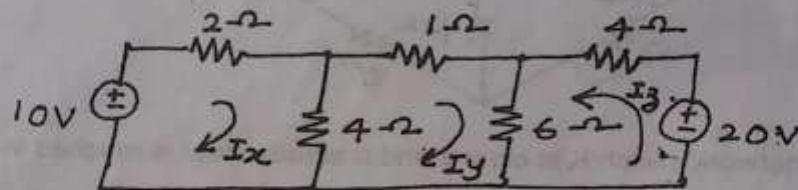
(b) Using graph theory find mesh currents Ix, Iy and Iz —



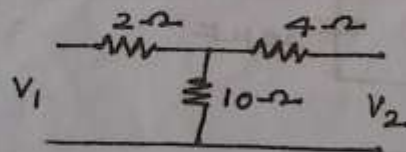4. (a) Find transmission parameters of the two networks A and B if they are connected in cascade —




Network (A)

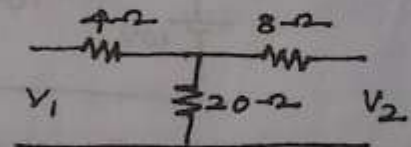

Network (B)

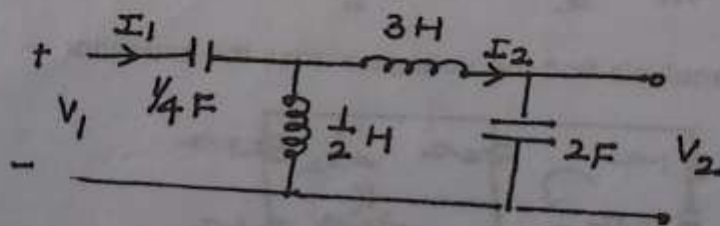
(b) Calculate V_2/V_1 , I_2/I_1 , input impedance and transfer function V_2/I_1 for given ladder network.



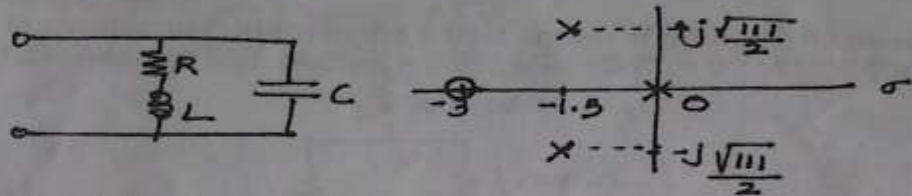
5. (a) The network shown below has the impedance form —

$$z(s) = \frac{K(s - z_1)}{(s - P_1)(s - P_2)}$$

If the poles and zeros of $z(s)$ have the pole zero plot as shown in figure (b) with $z(j\omega) = 1$. Find values of R , L and C —



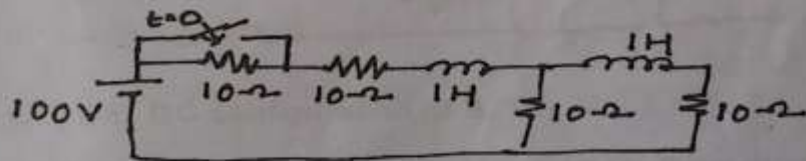- (b) (i) Define following terms :—
 (1) Gain Margin
 (2) Phase Margin
 (3) Gain cross-over frequency.
 (ii) Write short note on Significance of Initial Condition.
6. A designer requires the network with following data :—
 (a) Impedance function has simple poles at -2 and -6
 (b) It has simple zeros at -3 and -7
 (c) $z(0) = 20 \Omega$
 Find Foster I, Cauer I and Cauer II forms.
7. (a) In the network shown below switch K is closed at $t = 0$, a steady state having previous existed. Find the current in the resistor R_3 using Laplace.



- (b) If $i_L(0) = 10A$ in the circuit shown. Find $i_L(t)$ for $t > 0$.

