

S.E. (Biomedical) (Sem-III) May 2011

184-mk: 181H2-11.

Con. 3953-11.

Electrical Network Analysis & Synthesis

11/6/11

RK-1282


(3 Hours)

[Total Marks : 100

- N.B. (1) Question No. 1 is compulsory.
(2) Attempt any four questions out of remaining six questions.
(3) Assume any suitable data if required.
(4) Figures to the right indicates full marks.


1. (a) Draw the dual of the network.

5

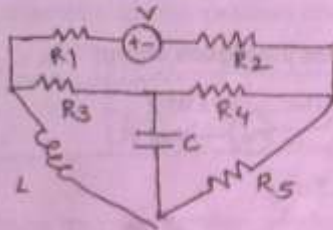

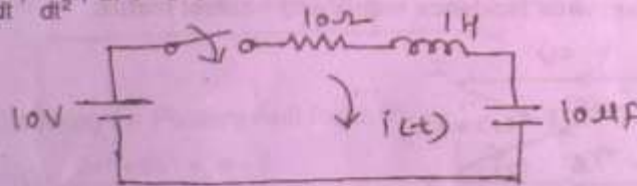
- (b) Write a short note on Initial condition and its significance. 5
(c) In the network shown, switch is closed. Assuming all initial conditions as zero, 5

find i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$, at $t=0^+$.




- (d) Find nodal voltages in the circuit shown in figure :-


5

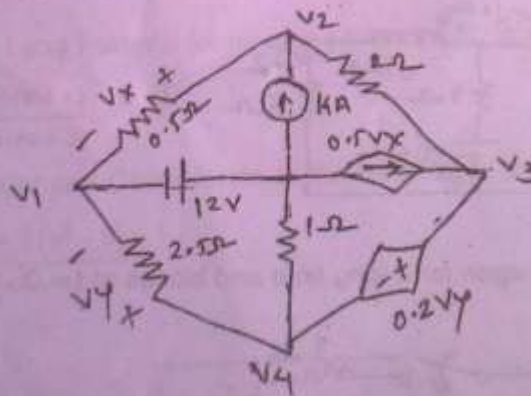

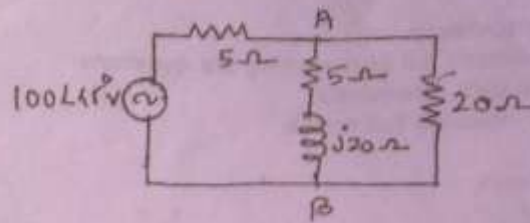
2. (a) For the network shown in figure find voltage V_{AB} :-



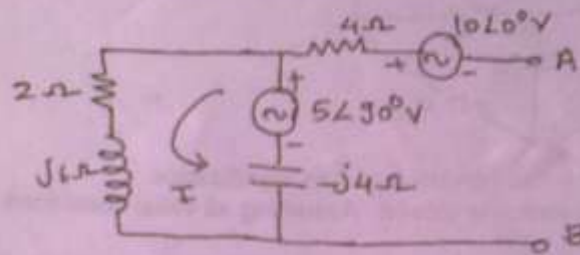
(b) Obtain Thevenin's equivalent network for the figure shown :-



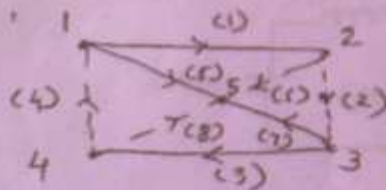
3. (a) For the graph shown, write incidence matrix and f-cutset matrix.




(b) Find I_2 by mesh analysis :-

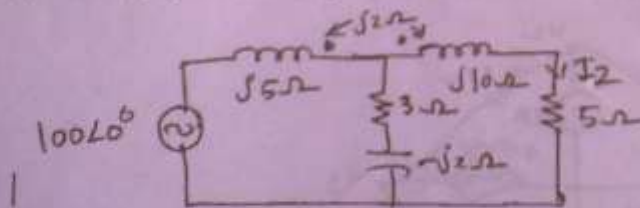

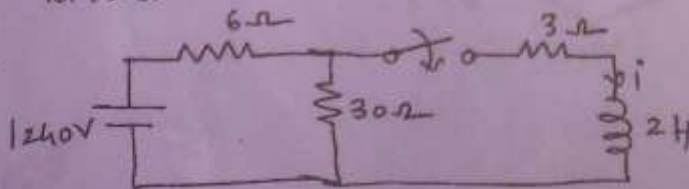
4. (a) The switch in figure is open for a long time and closes at $t = 0$. Determine $i(t)$ for $t > 0$.



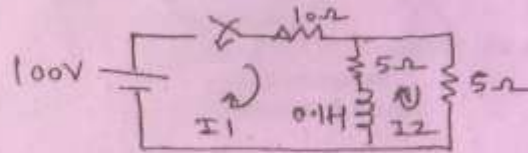
- (b) For the circuit shown in figure. Find currents $i_1(t)$ and $i_2(t)$ which results when 10 switch is closed at $t = 0$. 10



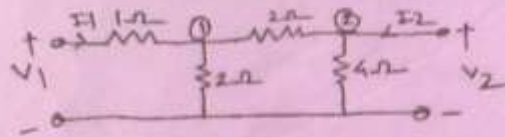5. (a) Determine Y parameter for the network shown — 10



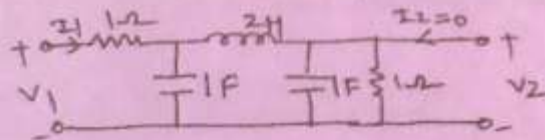- (b) Determine voltage transfer function $\frac{V_2}{V_1}$ for the network. 10



6. (a) Test the following for Positive real function: — 10

$$F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$$

- (b) (i) State and derive maximum power transfer theorem for d.c. circuit. 5
(ii) Explain gain crossover frequency and phase margin. 5

7. (a) Find the Foster I and Foster II forms of the following R_L impedance function: — 10

$$Z(s) = \frac{(s+1)(s+4)}{(s+5)(s+3)}$$

- (b) Realise the Foster and Cauer forms of the following impedance function: — 10

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$